
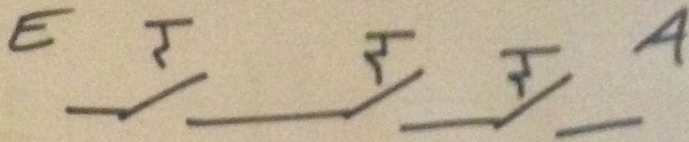


Und

NAND

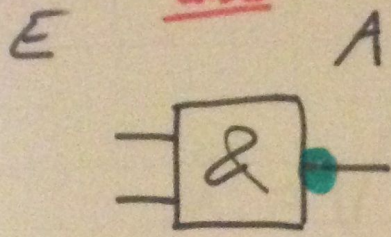


$$A = E_1 \wedge E_2$$

E_1	E_2	A	\bar{A}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

ODER

NOR


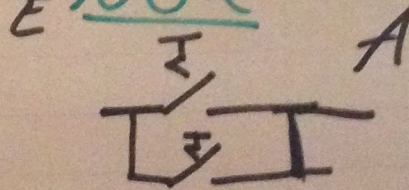


$$Y = \bar{I}_1 \vee \bar{I}_2$$


\bar{I}_1	\bar{I}_2	Q	\bar{Q}
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Negation

EXOR

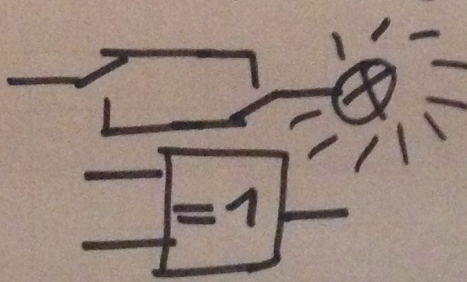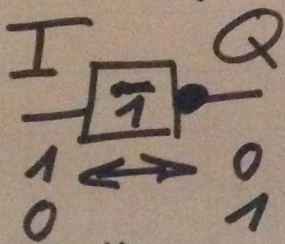

\bar{I}_1	\bar{I}_2	Q	\bar{Q}
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

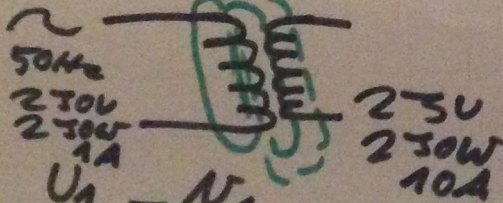

$$\frac{U_1}{U_2} = \frac{N_1}{N_2}$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$\frac{230V}{11,5V} = \frac{600}{?} \Rightarrow N \cdot \sqrt{I} = 20$$

$$\frac{230V}{6V} = \frac{1,15}{?}$$

$$N_2 = 5000 \text{dg}$$

$$\frac{2,5A}{1 \text{mm}^2} = \frac{?}{0,19 \text{mm}^2}$$

$$\ddot{M} = \sqrt{\frac{Z_p}{Z_s}}$$

$$| \quad |^2$$

$$\ddot{M}^2 = \frac{Z_p}{Z_s}$$

$$| \quad | \cdot Z_s$$

$$Z_p = \ddot{M}^2 \cdot Z_s$$

$$Z_p = 0,25^2 \cdot 768 \Omega$$

$$Z_p = \underline{\underline{48 \Omega}}$$